


Clocks, Registers, Other Hardware

CS 2130: Computer Systems and Organization 1
September 12, 2025

Announcements

- Quiz 2 out later today, due Sunday at 11:59pm
- Homework 1 due Monday
- Homework 2 available Monday

Ripple-Carry Adder

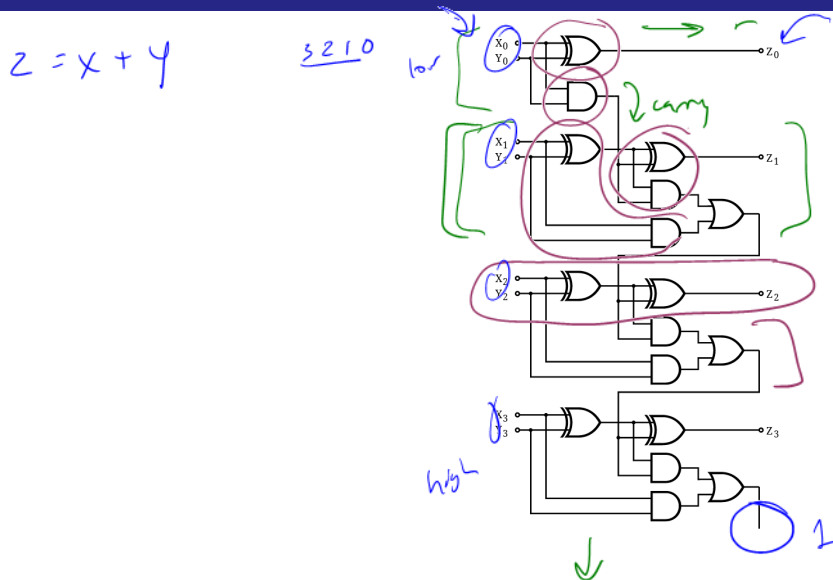


Ripple-Carry Adder

$$Z = x - y$$


$$Z = x + (-y)$$

↑
~
+1


$$Z = x + (\sim y) + 1$$

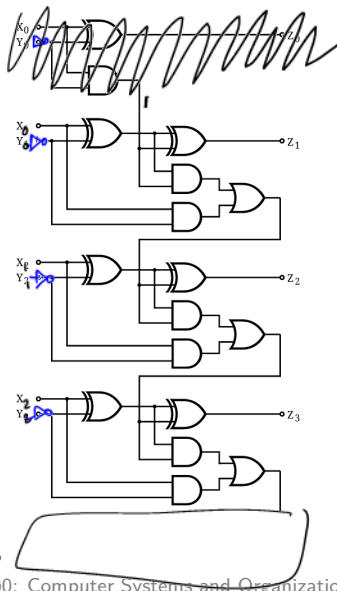


What does this circuit do?

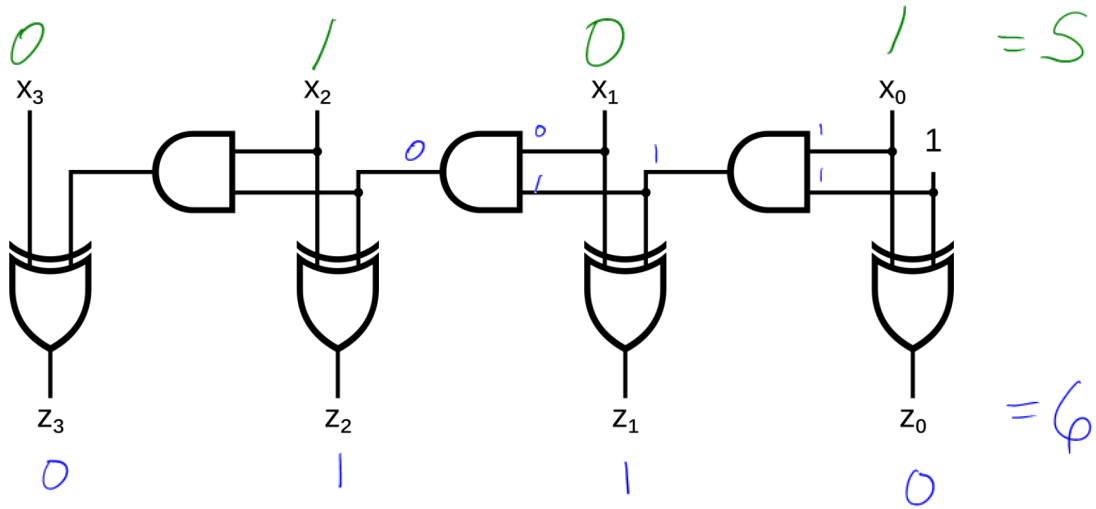


What does this circuit do?

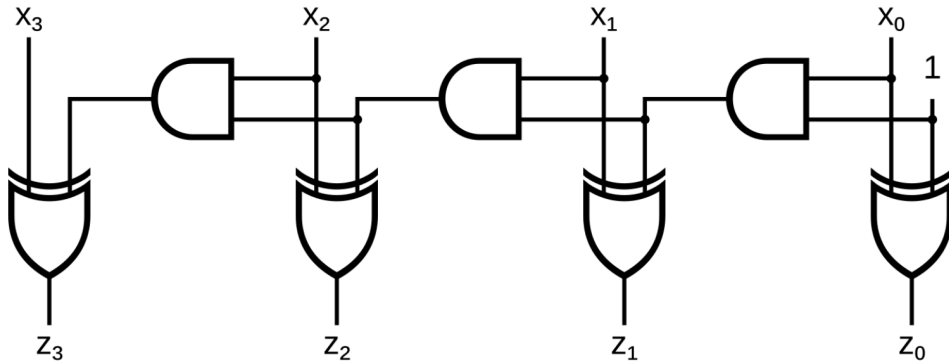


Increment Circuit

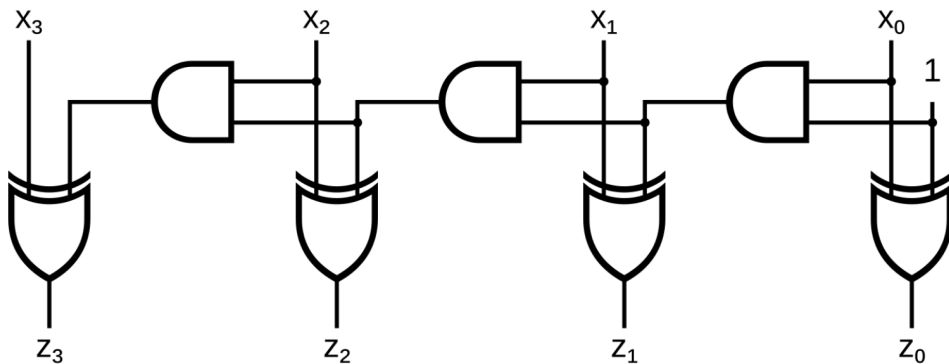

Building a Counter

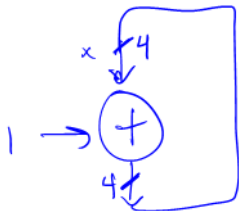


Building a Counter

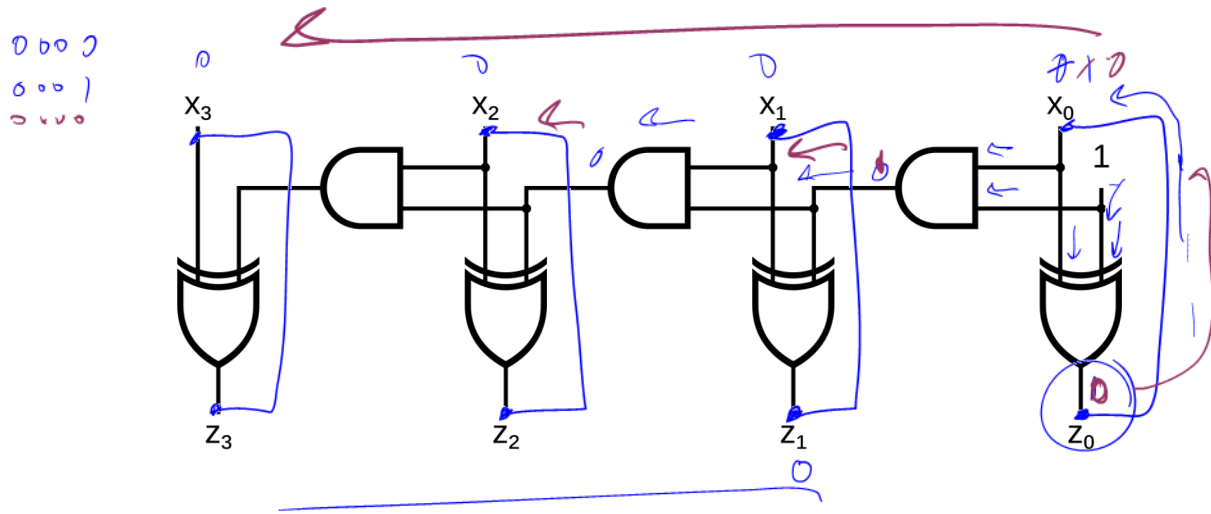


Gate Delay


What happens when I change my input?

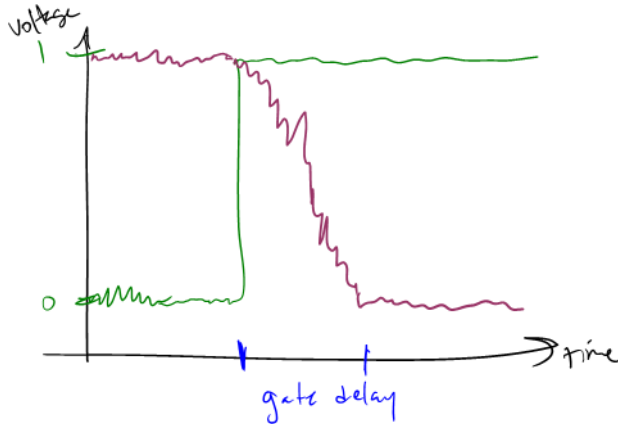


Building a Counter - Waiting

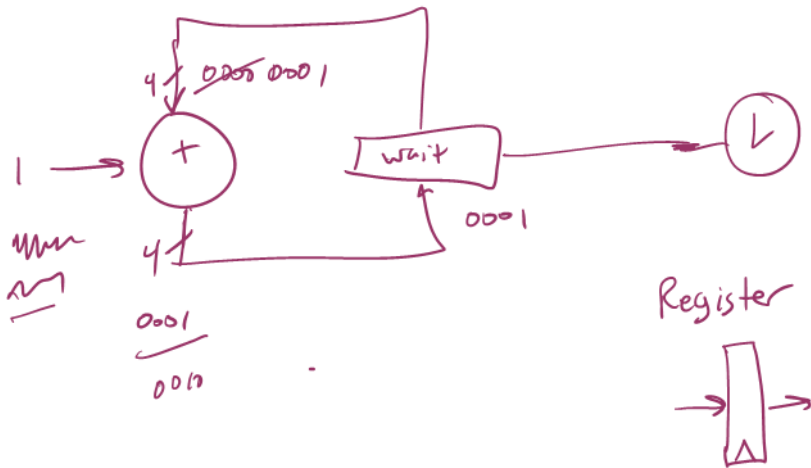


1-bit Register Circuit

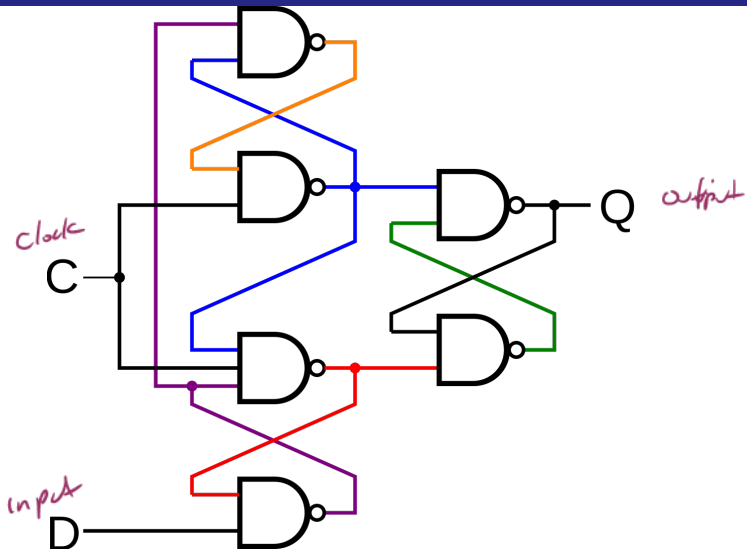


1-bit Register Circuit

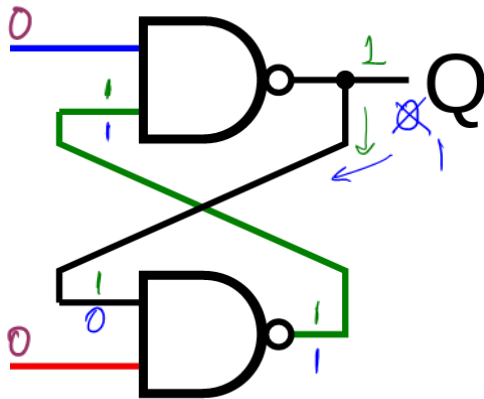


1-bit Register Circuit

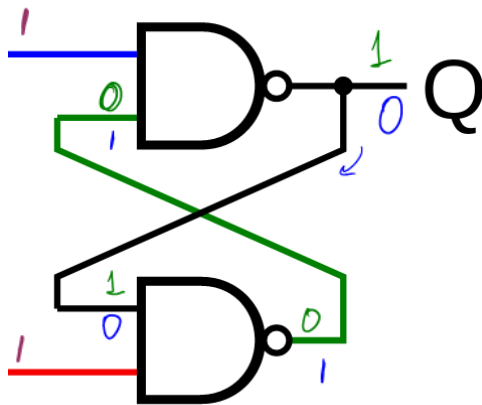


1-bit Register Circuit

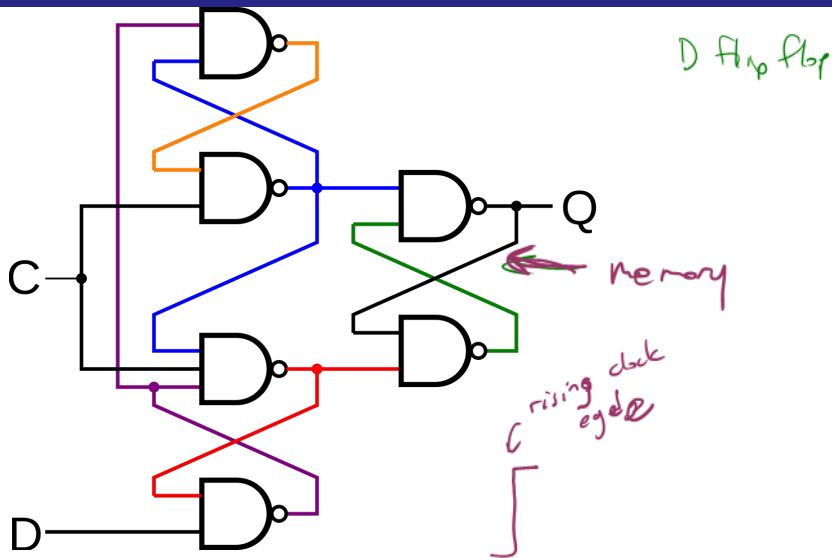


Building a Counter

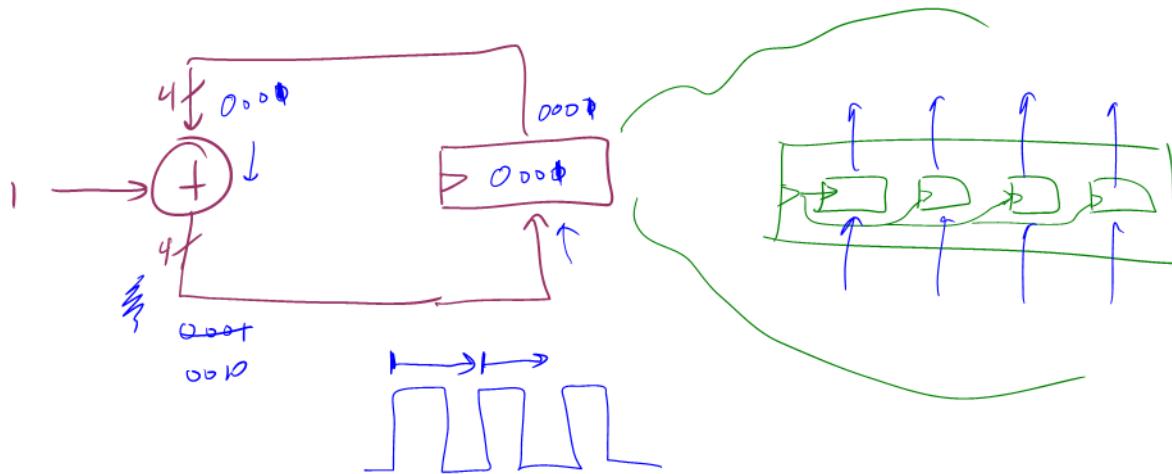

Another Circuit

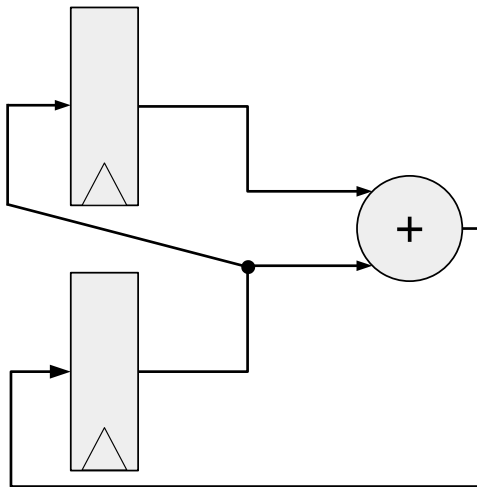

Another Circuit

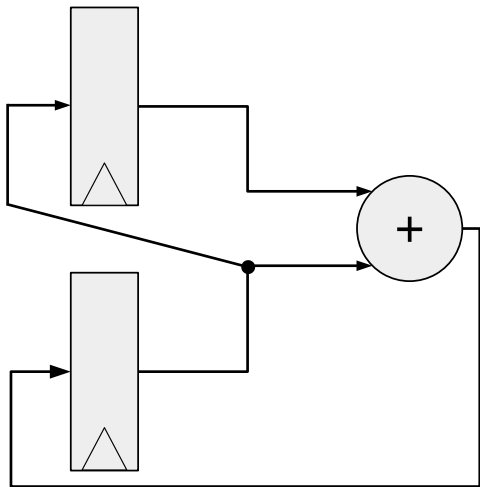

Common Model in Computers

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know: $\&$, $|$, \wedge , \sim
- Operations we can build from gates: $+$, $-$
- Others we can build:

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know: $\&$, $|$, \wedge , \sim
- Operations we can build from gates: $+$, $-$
- Others we can build:
- Ternary operator: $?$ $:$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?
 $x = 1$
 $x = 0$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?
 $x = 1$
 $x = 0$
- **Single assignment:** each variable can only be assigned a value once